

lab 1

Build an 8-bit ALU with Logisim

M. Briday

October 20, 2020

1 Objective

The objective of the lab is to build an ALU from basic logic elements, using the *logisim*¹ tool.

This lab is split in 3 parts:

- build a very basic 1-bit full adder, using only logic gates;
- from this adder, construct a 8-bit basic adder;
- build an ALU that can add, subtract and perform some basic logical operations, and outputs a status of the operation.

A sequential 8x8 hardware multiplier is eventually implemented using the adder and shift registers.

2 Adder

2.1 1-bit adder

A full adder has in addition to its 2 inputs a and b , the management of the carry (both input and output), as in Fig. 1.

- ▷ give the truth table of the 1-bit full adder;
- ▷ give the 2 equations of the outputs s_0 and c_1 ;

With logisim, draw the schematic of these 2 signals. You may use the operators in the *gates* section. The input/outputs should be defined in *wiring->Pin*. You can define the external appearance of your model:

¹You can download the *Italian fork* that adds copy/paste, zoom,... at <https://sourceforge.net/projects/logisimit/>. Logisim is cross-platform and requires Java.



 


Figure 1: 1-bit full adder. c_i is the carry

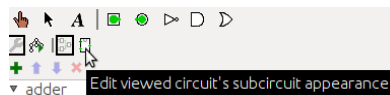

 Then, you can rename your current circuit, and add another one:



- ▷ test your solution with different inputs. On the *main* circuit, connect the inputs to wiring->Constant values, and outputs to Wiring->Probe.

Note that your test should consider the 1-bit adder as a black box!


2.2 8-bit Ripple-Carry adder

Using this 1-bit adder component, we now create a 8-bit adder component, as in Fig. 2: the output carry c_{i+1} of the 1-bit adder A_i is connected to the input carry of A_{i+1} .

We will have to use a 8-bits input pin (Wiring->Pin) and a splitter to change a 8-bit bus into 8 1-bits wires (Wiring->Splitter).

Note: instead of long wires, you can use a *tunnel* (Wiring->Tunnel) to make a wire connection between 2 tunnels with the same name.

- ▷ implement the 8-bits adder;
- ▷ with a new circuit, connect *constant* and *probes* correctly and test the adder as a black box as in the screenshot:

 

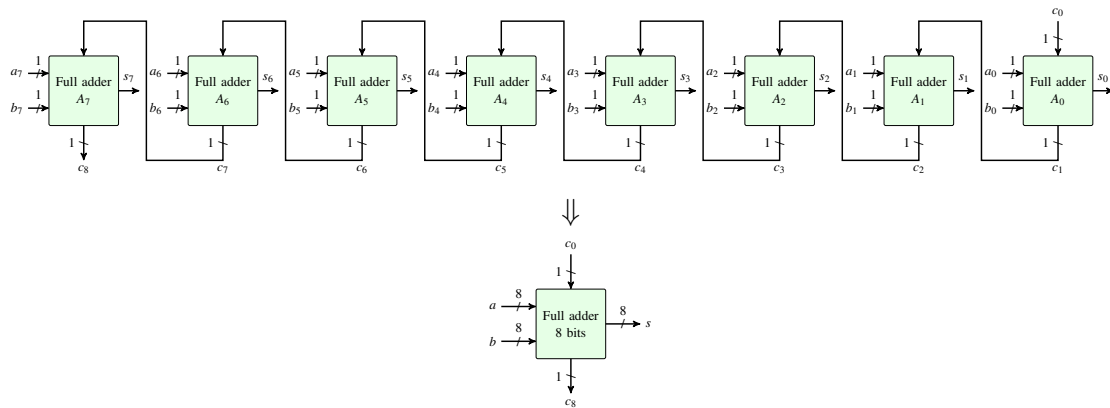


Figure 2: 8-bit full adder. c_i is the carry

3 ALU

Most of the ALU is the adder, and we add some logic functions (AND, OR, ...). All these functions are performed simultaneously, and a multiplexer before the output selects the appropriate operation.

 


Figure 3: 8-bit ALU.

op is a 3-bits input signal that selects the operation:

0. addition

1. subtraction

2. and

3. or

4. not: $\sim a$

5. xor

6. shift left²: $a \ll b$

7. shift right: $a \gg b$

²Most modern processor implements a multi-bit shift, but the Microchip AVR for instance does not!

status is a 4-bits output signal that gives the common status of an ALU:

0. Negative
1. Zero

2. overflow: the result has an incorrect sign, *i.e.* the sum of 2 positive numbers is a negative number.

3. Carry: the 9th bit of an operation.

The *c* 1-bit signal is an input carry for the ADC (Add with carry) instruction only. We can't use the actual carry bit, because our implementation has no flip-flop.

Notes:

- the subtraction may use the adder and use the properties of the two's complement : $-b = \sim b + 1$.
- you can use Arithmetic->Shifter and multiplexers in Plexers.
- ▷ Implement the different operations, with the output status.

3.1 Basic extension: Multiplier

The *arithmetic shift right* perform a shift with a sign extension: If the value is negative, then the bits added at left are 1 instead of 0.

- ▷ Add Arithmetic shift right operation (instead of not)

4 One step further... a multiplier!

The multiplier works in the same way as in the decimal way learnt at school, with the calculation of partial products:

456	1001	(B)
X 123	X 0101	(A)
<hr style="border-top: 1px dashed black;"/>		
1368	1001	
912.	0000.	
456..	1001..	
<hr style="border-top: 1px dashed black;"/> 56088	0000...	
	<hr style="border-top: 1px dashed black;"/> 0101101	

We implement here an hardware multiplier (Fig. 4) as a sequential operator which adds either B or 0 to the product (a partial product) and performs shifts at each step. If A and B require *n* bits, then the product is a *2n* bits value.

- P is set initially to 0

 


Figure 4: Multiplier

- for each step (n steps):
 - if the lsb of A is 1, then B is added to P. The sum is placed back in P.
 - P and A are shifted right, with the carry-out of the sum being moved into the MSB of P, the LSB of P moved to the MSB of A, and the LSB of A shifted out.

After n steps, the products appears in register P and A, with A holding the low order bits.

The circuit is sequential and needs to perform shifts and adds one after the other. We can use for the registers A, P, B and the carry-out a shift register as defined in Fig. 6:

- If load is set when there is a rising edge on clk, then S is copied into P
- If shift is set when there is a rising edge on clk, then the content of P is shifted: new input bit on the left blue wire (MSB), output bit on the red wire at right (LSB)
- At each time, the value of the register can be read (signal P).
- The value of the register can be updated during simulation using the 'hand' tool and a click on a value.

To generate the clocks load and shift, we use a simple frequency divider with a flip-flop:

 


Figure 5: Shift register

 


Figure 6: clocks shift and load generation using a flip-flop